
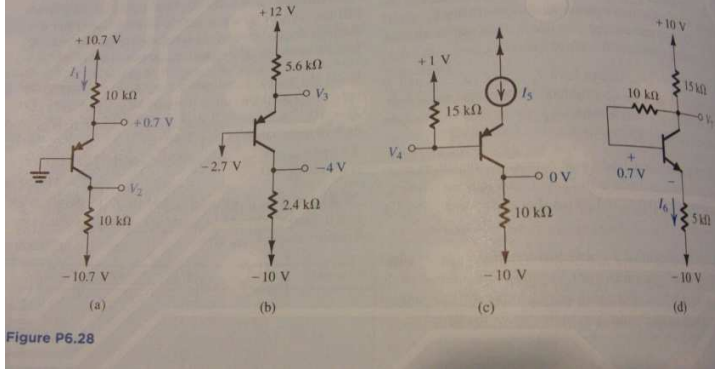


Exercices #4

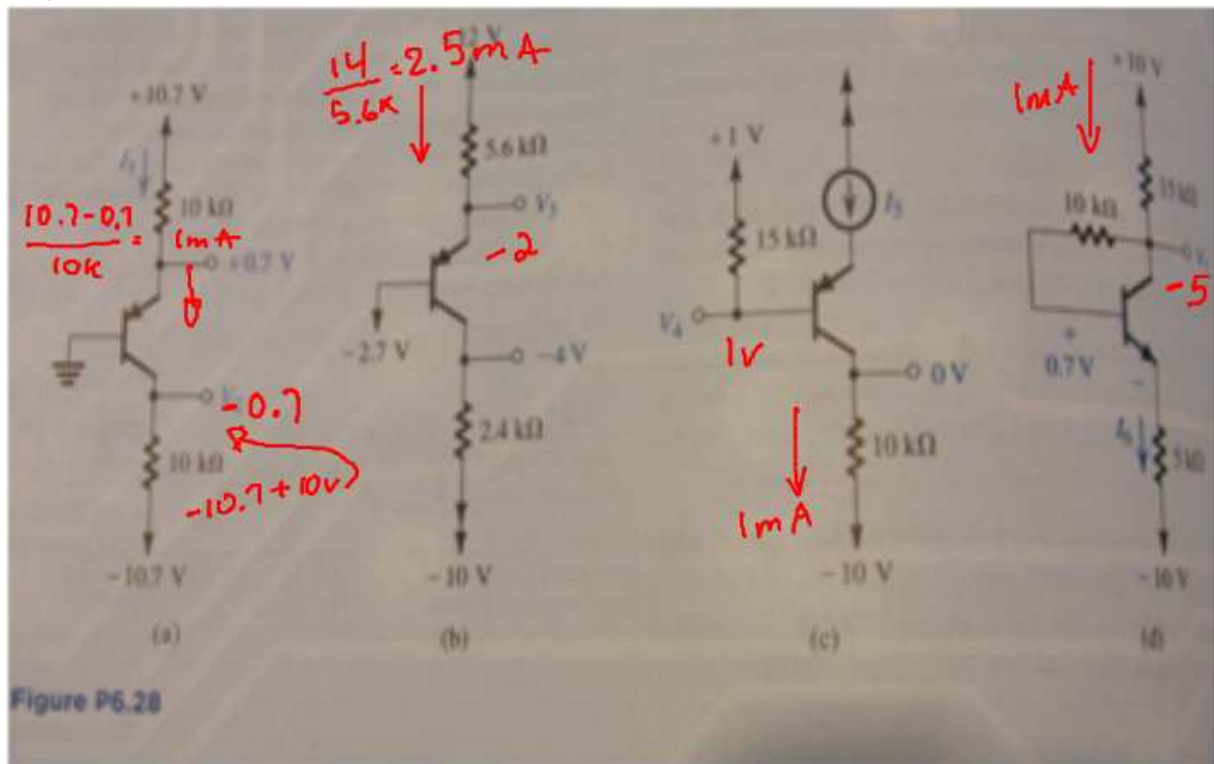6.28 For the circuits in Fig. P6.28, assume that the transistors have very large β . Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.



Quand on dit que le β est grand, ca veut simplement dire qu'il n'y a pas de courant qui entre dans la base. Donc, $I_E = I_C$.



6.29 Measurements on the circuits of Fig. P6.29 produce labeled voltages as indicated. Find the value of β for each transistor.

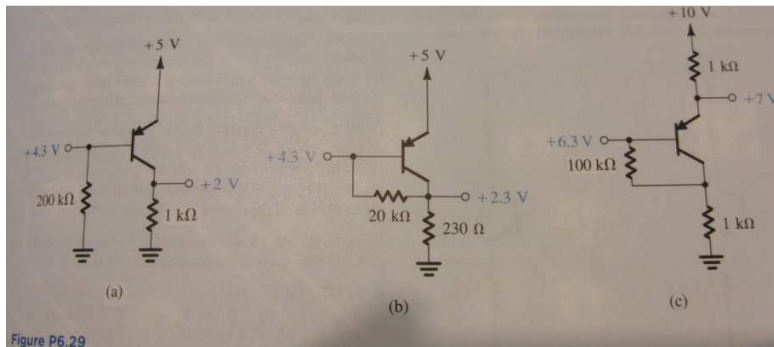


Figure P6.29

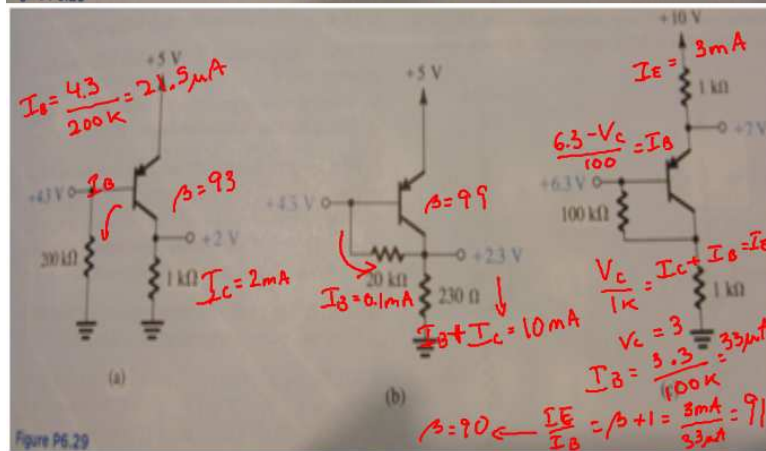


Figure P6.29

6.35 For each of the circuits shown in Fig. P6.35, find the emitter, base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8 \text{ V}$ independent of current level.


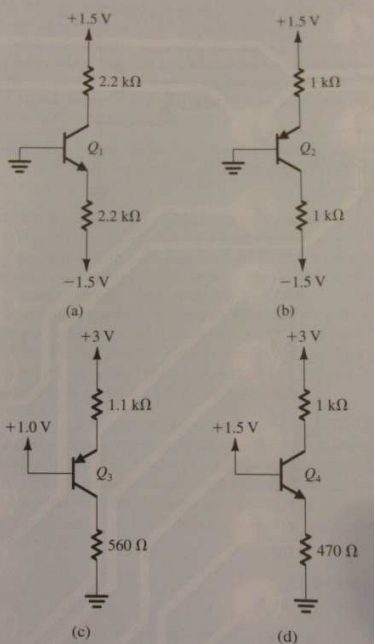


Figure P6.35

6.35 For each of the circuits shown in Fig. P6.35, find the emitter, base, and collector voltages and currents. Use $\beta = 50$, but assume $|V_{BE}| = 0.8 \text{ V}$ independent of current level.

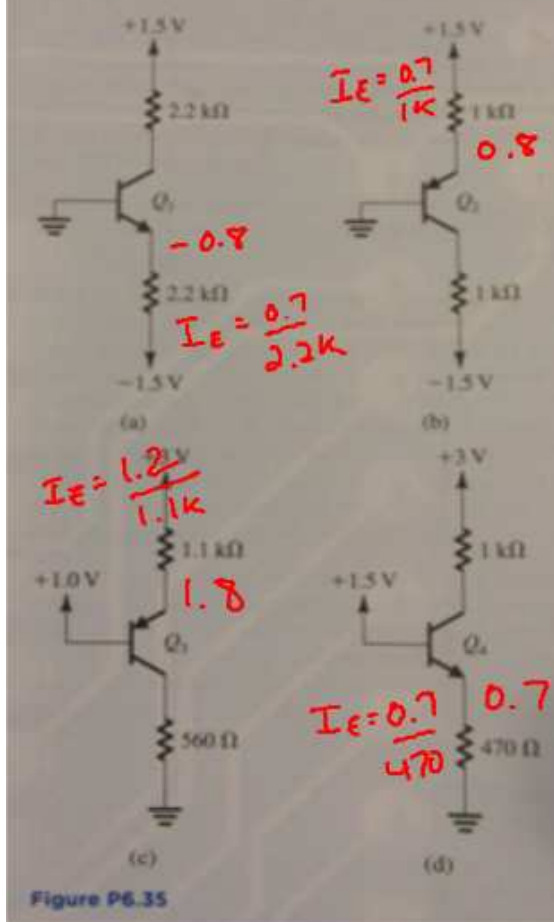

a)
 $i_e = 318 \mu\text{A}$
 $i_c = \beta / (\beta + 1) i_e = 312 \mu\text{A}$
 $v_c = v_{cc} - i_c \cdot r_c = 0.814$

b)
 $i_e = 0.7 \text{ mA}$
 $i_c = 686 \mu\text{A}$
 $v_c = -0.814$

c)
 $i_e = 1.09 \text{ mA}$
 $i_c = 1.07 \text{ mA}$
 $v_c = 0.61$

d)
 $i_e = 1.49 \text{ mA}$
 $i_c = 1.46 \text{ mA}$
 $v_c = 1.54$

6.62 For the circuits in Fig. P6.62, find values for the labeled node voltages and branch currents. Assume β to be very high.


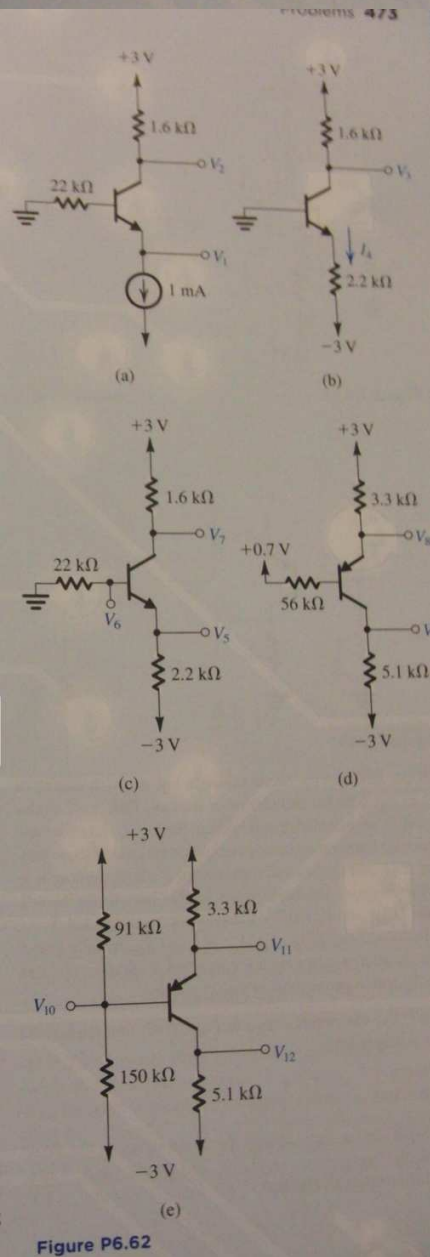


Figure P6.62

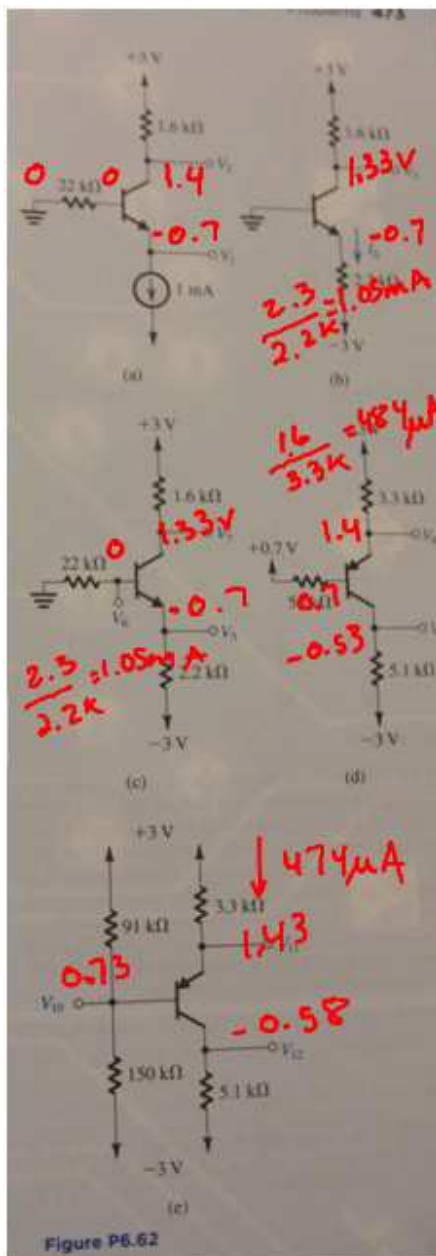

*6.67 For the circuit shown in Fig. P6.67, find the labeled node voltages for:

- (a) $\beta = \infty$
- (b) $\beta = 100$

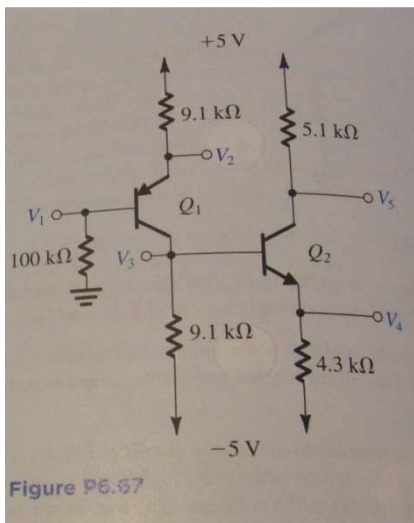


Figure P6.67

β infini

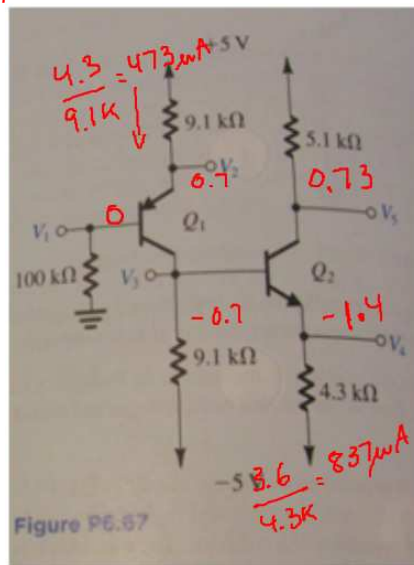


Figure P6.67

$\beta=100$

Transistor Q1:

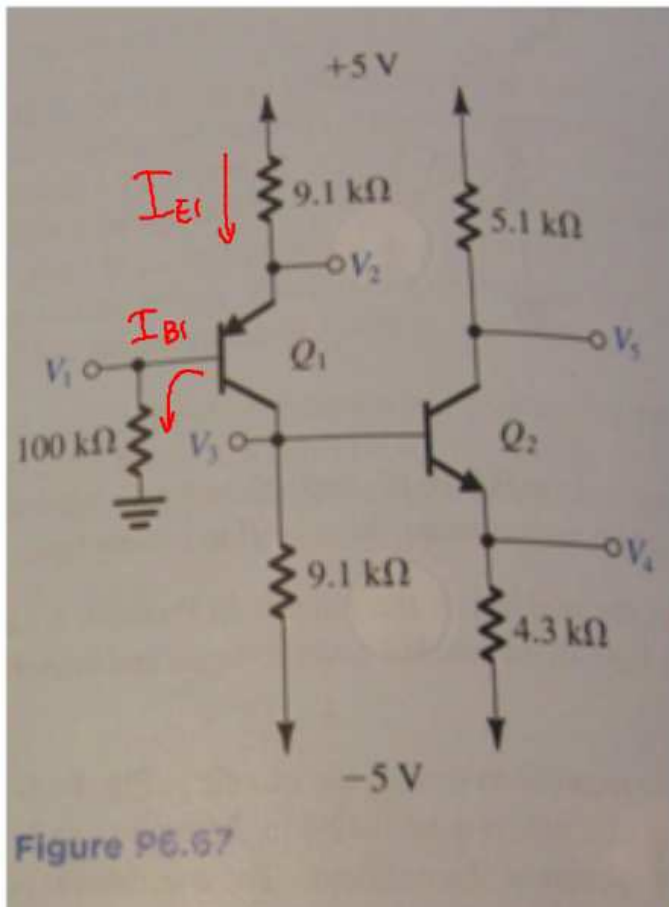


Figure P6.67

Transistor Q2:

$$V_{B1} = I_{B1} \cdot 100k$$

$$I_{E1} = (\beta + 1) I_{B1} = \frac{5 - (V_{B1} + 0.7)}{9100}$$

$$(\beta + 1) I_{B1} = \frac{5 - (I_{B1} \cdot 100k + 0.7)}{9100}$$

$$I_{B1} = 4.2 \mu A$$

$$I_{E1} = 426 \mu A$$

$$V_2 = 5 - 9100 \cdot I_{E1} = 1.12 V$$

$$V_1 = 0.42 V$$

$$I_{C1} = 420 \mu A$$

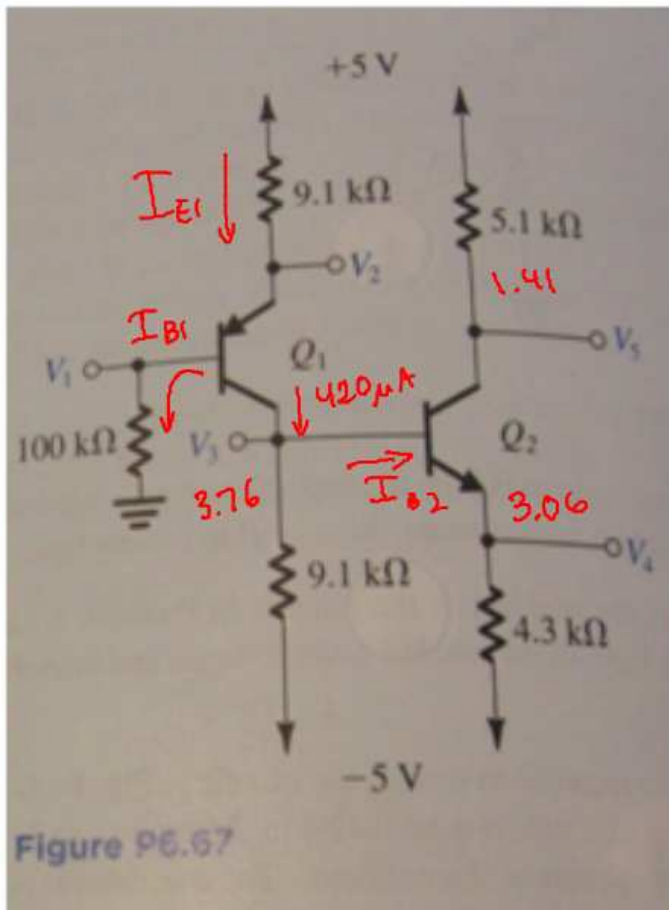


Figure P6.67

$$I_{C1} = 420 \mu\text{A}$$

$$I_{C1} = \frac{V_{B2}}{9.1\text{k}} + I_{B2}$$

$$I_{E2} = \frac{V_{B2} - 0.7}{4.3\text{k}} = (\beta + 1) I_{B2}$$

$$I_{B2} = 7.04 \mu\text{A}$$

$$V_{B2} = 3.76\text{V}$$

$$V_{E2} = 3.06\text{V}$$

$$V_{C2} = 5 - I_{C2} \cdot 5100$$

$$= 5 - 704 \mu\text{A} \cdot 5100$$

$$= 1.41$$